

Road Lights - Fault Finding - Understanding a basic electrical circuit.



21 Watt indicator bulb

Left: A simple circuit showing the indicator (turn signal) bulb.

For simplicity all switches in the tow vehicle have been omitted.

One 'connector' of the 13 Pin Plug

One 'connector' of the 13 Pin Socket

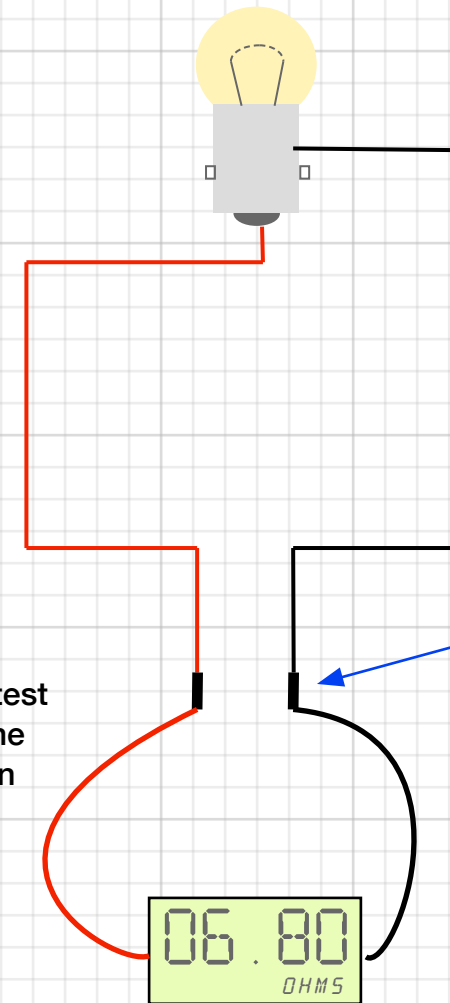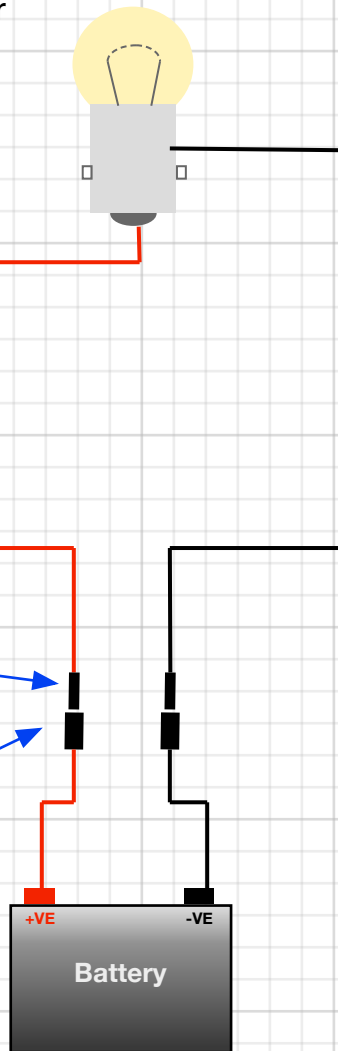

Right: How we would test the circuit shown on the left with a multimeter in the caravan or trailer.

